

CS224

Lab 4

Sec. 5

Suleyman Hanyyev

21901009

Part 1:

A)

Location(hex)	Machine Instruction(hex)	Assembly Equivalent
0	20020005	addi \$v0, \$zero 5
8'h04	"2003000c"	addi \$v1, \$zero, 12
8'h08	"2067fff7"	addi \$a3, \$v1, -9
8'h0c	"00e22025"	or \$a0, \$a3, \$v0
8'h10	"00642824"	and \$a2, \$v1, \$a0
8'h14	"00a42820"	add \$a1, \$a0, \$a1
8'h18	"10a7000a"	Beq \$a1, \$a3, target (pc+44)
8'h1c	"0064202a"	Slt \$a0, \$v1, \$a0
8'h20	"10800001"	beq \$a0, \$zero, pc+ 8
8'h24	"20050000"	addi \$a1, \$zero, 0
8'h28	"00e2202a"	slt \$a0,\$a3,\$v0
8'h2c	"00853820"	add \$a3,\$a1,\$a2
8'h30	"00e23822"	sub \$a3,\$a3,\$v0
8'h34	"ac670044"	sw \$a3,68(\$v1)
8'h38	"8c020050"	lw \$v0,80(\$zero)
8'h3c	"08000010"	j 0x80000040
8'h40	"001f6020"	add \$t4,\$zero, \$ra
8'h44	"0c000012"	jal 0x80000048
8'h48	"ac020054"	sw \$v0,84(\$0)
8'h4c	"00039042"	srl \$s2,\$v1,0x1
8'h50	"03E00008"	jr \$ra

F)

i) it corresponds to RD2.

ii) I think it is because in one clock cycle it becomes AluSrcB and the actual writedata is no longer needed and therefore is undefined.

iii) Because it is only used in lw function.


iv) To the result out of ALU.

v) it becomes aluout

G)

i) Yes, we will need to make alusrcA mux 4:1 not 2:1. This is because the mux has to know whether it should take RD1 or the rs.

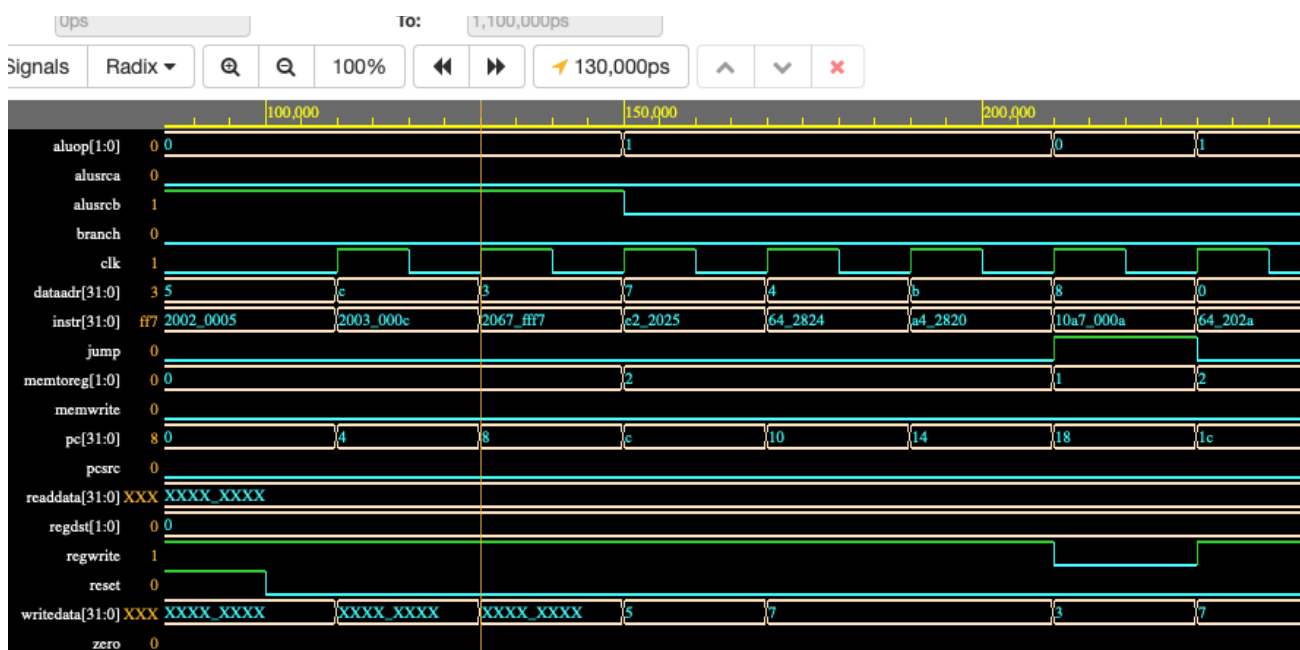ii) I don't think we need to modify anything. Part 2:



revert to EPWave opening in a new browser window, set that option on your user page.

Part 2:

A) IM[PC] , RF[Instr(25:21)] RF[Instr(20:16)]

$$\text{ALUResult} = \text{RF}[\text{rs}] - \text{RF}[\text{rt}]$$

if( zero = 0) then PC <- PC+4 + BTA

B) I did not make any additional changes, simply because I didn't think I needed them. I will use the  $a < b$  operation in the alu and if it is less, the flag zero will be 1 and I can use that for the BTA

C)

Instruction	Opcod e	RegW rite	RegDs t	ALUSr cA	ALUSr cB	Branc h	MemW rite	MemT oReg	ALUO p	Jump
lw	100011	1	00	0	1	0	0	01	00	00
sw	101011	0	X	0	1	0	1	XX	00	'00
beq	00010 0	0	X	0	0	1	0	01	01	00
addi	00100 0	1	00	0	1	0	0	00	00	00
j	00001 0	0	X	X	X	X	0	XX	XX	01
jal	00001 1	1	10	X	X	X	0	10	XX	01
ble	'01010 1	0	XX	0	0	1	0	XX	11	00
srl	00000 0	1	01	0	0	0	0	00	10	00
R	00000 0	1	'01	0	0	0	0	00	10	00

ALU Decoder:

AluOP	Funct	ALUcontrol
00	X	010(add)
01	X	110(subtract)
11	X	111(slt)
XX	100000 (add)	010(add)
XX	100010 (sub)	110(subtract)
XX	100100 (and)	000(and)
XX	100101 (or)	001(or)
XX	101010 (slt)	111(slt)
XX	000010 (srl)	011(srl)